

Faculty of Science

B. Sc (Electronics) I-Year, CBCS-I Semester Regular Examinations, Dec/Jan 2019-20

PAPER: CIRCUIT ANALYSIS

Time: 3 Hours

Max Marks: 80

Section-A


I. Answer **EIGHT** from the following questions (**Two from each part**) (8x4=32 Marks)

PART-A

1. Write a short note on J operator.
2. Differentiate voltage and current sources.
3. The peak value of a sine wave is 1V. Find average and rms values.

PART-B

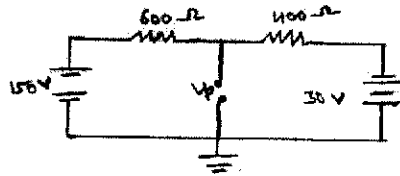4. State superposition theorem and draw the circuit diagram.
5. State reciprocity theorem and list its applications.
6. Determine V_p by superposition in following circuit:



PART-C

7. Discuss about transient response of RL circuit with step input.
8. Obtain frequency response of a passive differentiating circuit.
9. Calculate time constant for circuit with $C=0.001\mu\text{F}$ and $R=1\text{M}\Omega$.

PART-D

10. Define Q factor and selectivity.
11. Write a note on functioning of electron gun.
12. Find f_r for a series circuit with $C=10\mu\text{F}$ and $L=16\text{H}$ and $R=5\Omega$.

Section-B


II. Answer the following questions (4x12=48 Marks)

13. (a) Define average and RMS values. Explain in detail about complex impedance and admittance.

(OR)

- (b) State and explain Kirchoff's voltage and current laws.

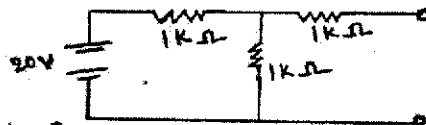14. (a) State and explain Thevenin's theorem. Find Thevenin equivalent circuit for following circuit:



(OR)

- (b) State and explain Maximum power transfer theorem. Give its applications.

15. (a) Obtain frequency response of an RC circuit.

(OR)

- (b) What are different types of filters? Obtain frequency response of a high pass filter.

16. (a) Obtain expression for resonant frequency of a RLC parallel resonance circuit.

(OR)

- (b) Explain working of a cathode ray tube.

